


Ejercicio 2012-8 E. Digital Selectividad.

mii	D	S ₁	S ₂	E ₁	E ₂	E ₃
0	0	0	0	1	1	1
1	0	0	1	0	1	1
2	0	1	0	1	0	1
3	0	1	1	1	1	0
4	1	0	0	1	1	1
5	1	0	1	1	1	1
6	1	1	0	1	1	1
7	1	1	1	1	1	1


$$E_1 = f(D, S_1, S_2) = \sum_3(0, 1, 2, 3, 4, 5, 6, 7)$$

$$E_2 = f(D, S_1, S_2) = \sum_3(0, 1, 3, 4, 5, 6, 7)$$

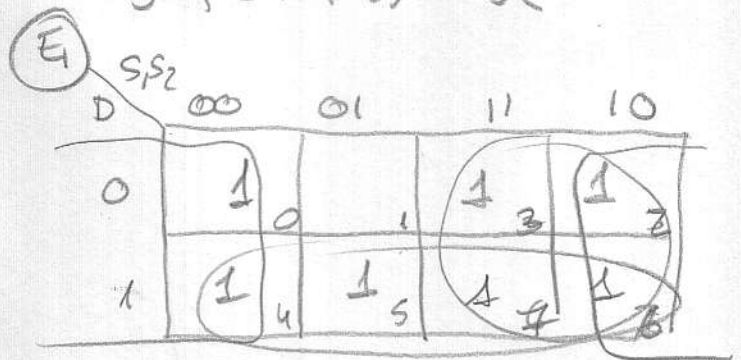
$$E_3 = f(D, S_1, S_2) = \sum_3(0, 1, 2, 4, 5, 6, 7)$$



$$E_1 = D + S_1 + \overline{S_2}$$

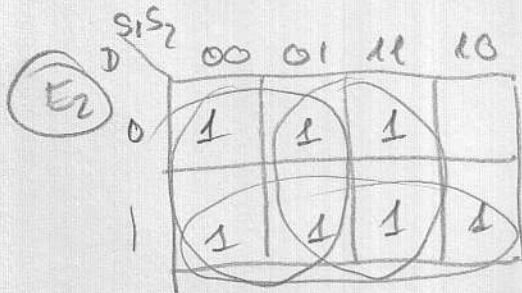

$$E_2 = D + \overline{S_1} + S_2$$

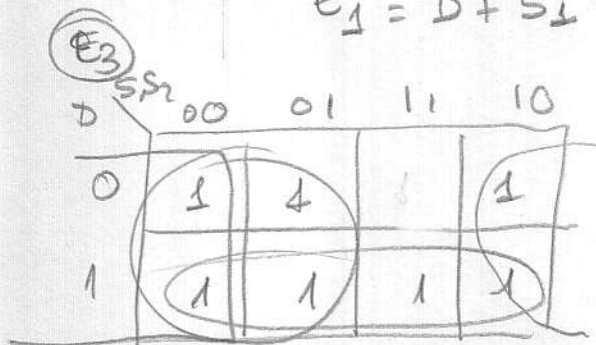

$$E_3 = D + \overline{S_1} + \overline{S_2}$$

