
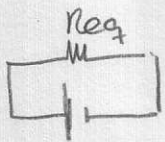
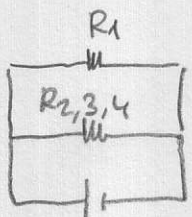
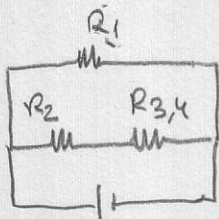


Ejercicio N° 39 (a).

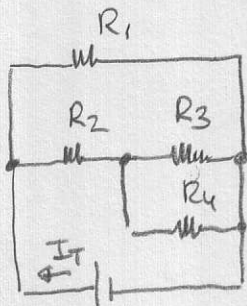

as Resist. equivalente:

$$\frac{1}{R_{3,4}} = \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{30} + \frac{1}{40} = \frac{30+40}{1200} = \frac{70}{1200}$$

$$R_{3,4} = \frac{1200}{70} = 17'14 \Omega$$

$$R_{2,3,4} = R_2 + R_{3,4} = 10 + 17'14 = 27'14 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_{2,3,4}} = \frac{1}{20} + \frac{1}{27'14} = \frac{27'14+20}{542'85} = \frac{47'14}{542'85}$$

$$\frac{1}{R_{eq}} = \frac{47'14}{542'85} \Rightarrow R_{eq} = \frac{542'85}{47'14} = 11'51 \Omega$$

b) $V_T = 100 \text{ V} \Rightarrow I_T = \frac{V_T}{R_{eq}} = \frac{100}{11'51} = 8'68 \text{ A}$

$$P_T = V_T \cdot I_T = 100 \cdot 8'68 = 868 \text{ W}$$

c) Como R_1 y $R_{2,3,4}$ están en paralelo $\Rightarrow V_T = V_{R_1} = V_{2,3,4} = 100 \text{ V}$

luego $\Rightarrow I_1 = \frac{V_1}{R_1} = \frac{100}{20} = 5 \text{ A}$

$$I_{2,3,4} = \frac{V_{2,3,4}}{R_{2,3,4}} = \frac{100}{27'14} = 3'68 \text{ A}$$

Como R_2 y $R_{3,4}$ están en serie $\Rightarrow I_{2,3,4} = I_2 = I_{3,4} = 3'68 \text{ A}$

luego: $V_2 = I_2 \cdot R_2 = 3'68 \cdot 10 = 36'8 \text{ V}$

$$V_{3,4} = I_{3,4} \cdot R_{3,4} = 3'68 \cdot 17'14 = 63'075 \text{ V}$$

Como R_3 y R_4 están en paralelo $\Rightarrow V_3 = V_4 = V_{3,4} = 63'075 \text{ V}$

luego $I_3 = \frac{V_3}{R_3} = \frac{63'075}{30} = 2'10 \text{ A}$

$$I_4 = \frac{V_4}{R_4} = \frac{63'075}{40} = 1'57 \text{ A}$$

las potencias:

$$P_1 = V_1 \cdot I_1 = 100 \cdot 5 = 500 \text{ W}$$

$$P_2 = V_2 \cdot I_2 = 36'8 \cdot 3'68 = 135'42 \text{ W}$$

$$P_3 = V_3 \cdot I_3 = 63'075 \cdot 2'10 = 132'45 \text{ W}$$

$$P_4 = V_4 \cdot I_4 = 63'075 \cdot 1'57 = 99'02 \text{ W}$$