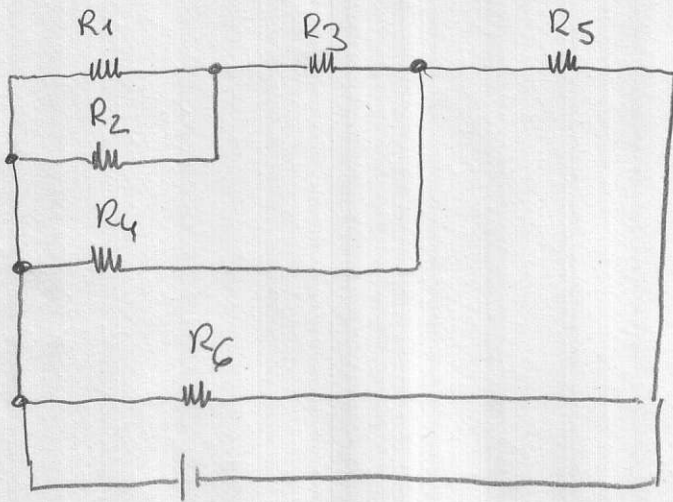


Ejercicio 39 (b).



Datos: $V_T = 200V$.

$R_1 = 10\ \Omega$





$R_2 = 40\ \Omega$

$R_3 = 20\ \Omega$

$R_4 = 50\ \Omega$

$R_5 = 30\ \Omega$

$R_6 = 60\ \Omega$

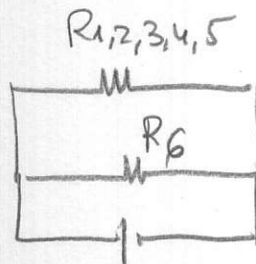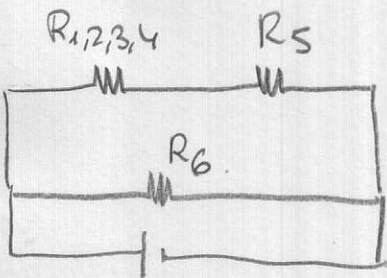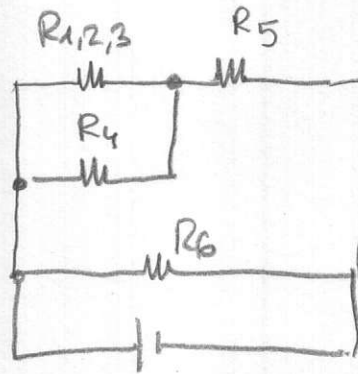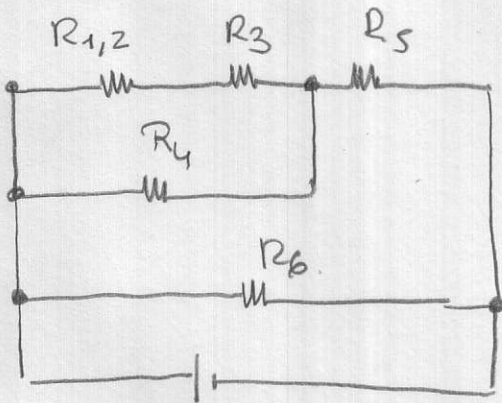

$$\frac{1}{R_{1,2}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{10} + \frac{1}{40} = \frac{40+10}{400} = \frac{50}{400} \Rightarrow R_{1,2} = \frac{400}{50} = 8\ \Omega$$

$$R_{1,2,3} = R_{1,2} + R_3 = 8 + 20 = 28\ \Omega$$

$$\frac{1}{R_{1,2,3,4}} = \frac{1}{R_{1,2,3}} + \frac{1}{R_4} = \frac{1}{28} + \frac{1}{50} = \frac{50+28}{28 \cdot 50} = \frac{78}{1400} \Rightarrow R_{1,2,3,4} = \frac{1400}{78} = 17'94\ \Omega$$

$$R_{1,2,3,4,5} = R_{1,2,3,4} + R_5 = 17'94 + 30 = 47'94\ \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_{1,2,3,4,5}} + \frac{1}{R_6} = \frac{1}{47'94} + \frac{1}{60} = \frac{60+47'94}{47'94 \cdot 60} = \frac{107'94}{2876'4} \Rightarrow R_{eq} = 26'64\ \Omega$$

$$I_T = \frac{V_T}{R_{eq}} = \frac{200}{26.64} = 7.5 \text{ A}$$

Como R_6 y $R_{1,2,3,4,5}$ están en paralelo $\Rightarrow V_T = V_{1,2,3,4,5} = V_6 = 200 \text{ V}$.

$$\text{luego } \Rightarrow I_{1,2,3,4,5} = \frac{V_{1,2,3,4,5}}{R_{1,2,3,4,5}} = \frac{200}{47.94} = 4.17 \text{ A}$$

$$I_6 = \frac{V_6}{R_6} = \frac{200}{60} = 3.33 \text{ A}$$

Como $R_{1,2,3,4}$ y R_5 están en serie $\Rightarrow I_{1,2,3,4} = I_5 = I_{1,2,3,4,5} = 4.17 \text{ A}$

$$\text{luego } \Rightarrow V_{1,2,3,4} = I_{1,2,3,4} \cdot R_{1,2,3,4} = 4.17 \cdot 17.94 = 74.84 \text{ V}$$

$$V_5 = I_5 \cdot R_5 = 4.17 \cdot 30 = 125.1 \text{ V}$$

Como $R_{1,2,3}$ y R_4 están en paralelo $\Rightarrow V_{1,2,3} = V_4 = V_{1,2,3,4} = 74.84 \text{ V}$

$$\text{luego } \Rightarrow I_{1,2,3} = \frac{V_{1,2,3}}{R_{1,2,3}} = \frac{74.84}{28} = 2.67 \text{ A}$$

$$I_4 = \frac{V_4}{R_4} = \frac{74.84}{50} = 1.4968 \text{ A}$$

Como $R_{1,2}$ y R_3 están en serie $\Rightarrow I_{1,2} = I_3 = I_{1,2,3} = 2.67 \text{ A}$

$$\text{luego } \Rightarrow V_{1,2} = I_{1,2} \cdot R_{1,2} = 2.67 \cdot 8 = 21.36 \text{ V}$$

$$V_3 = I_3 \cdot R_3 = 2.67 \cdot 20 = 53.4 \text{ V}$$

Como R_1 y R_2 están en paralelo $\Rightarrow V_1 = V_2 = V_{1,2} = 21.36 \text{ V}$.

$$\text{luego } I_1 = \frac{V_1}{R_1} = \frac{21.36}{10} = 2.136 \text{ A} \quad \# \quad I_2 = \frac{V_2}{R_2} = \frac{21.36}{40} = 0.534 \text{ A}$$

Las potencias: $P_T = V_T \cdot I_T = 200 \cdot 7.5 = 1500 \text{ W}$

$$P_1 = V_1 \cdot I_1 = 21.36 \cdot 2.136 = 45.62 \text{ W}$$

$$P_2 = V_2 \cdot I_2 = 21.36 \cdot 0.534 = 11.40 \text{ W}$$

$$P_3 = V_3 \cdot I_3 = 53.4 \cdot 2.67 = 142.57 \text{ W}$$

$$P_4 = V_4 \cdot I_4 = 74.84 \cdot 1.4968 = 112.02 \text{ W}$$

$$P_5 = V_5 \cdot I_5 = 125.1 \cdot 4.17 = 521.66 \text{ W}$$

$$P_6 = V_6 \cdot I_6 = 200 \cdot 3.33 = 666 \text{ W}$$